

DIGITAL SYSTEMS

PRACTICUM 5



By:

MUHAMMAD ROSYAD ADI PRATAMA


NIM: L200184044

INFORMATION TECHNOLOGY

FACULTY OF COMMUNICATION AND INFORMATICS

UNIVERSITY OF MUHAMMADIYAH SURAKARTA

Experiment 1

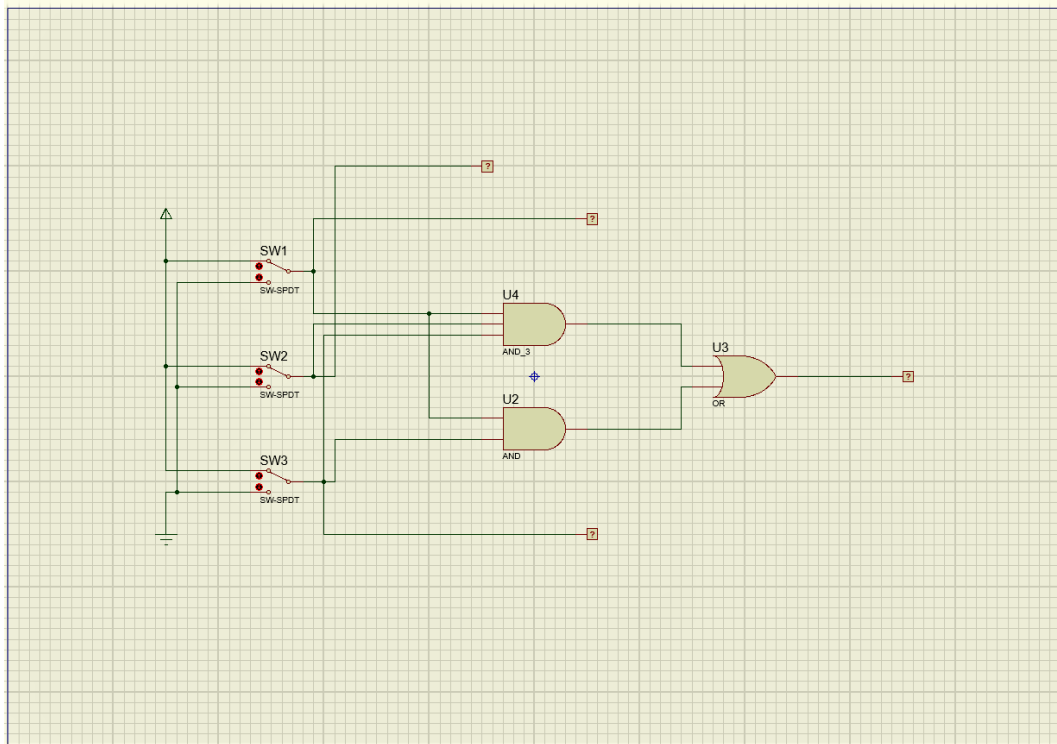

Picture 1.1. Logic gate combination

1. Boolean functions

$$F = ABC + AC$$

2. Truth table

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 |


3. Karnaugh map

| | | AB | | | |
|---|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| C | 0 | 0 | 0 | 0 | 0 |
| | 1 | 0 | 0 | 1 | 1 |
| | | | | | |

4. Boolean functions based on karnaugh map


$$F = AC$$

5. Logic gate combination based on new boolean functions

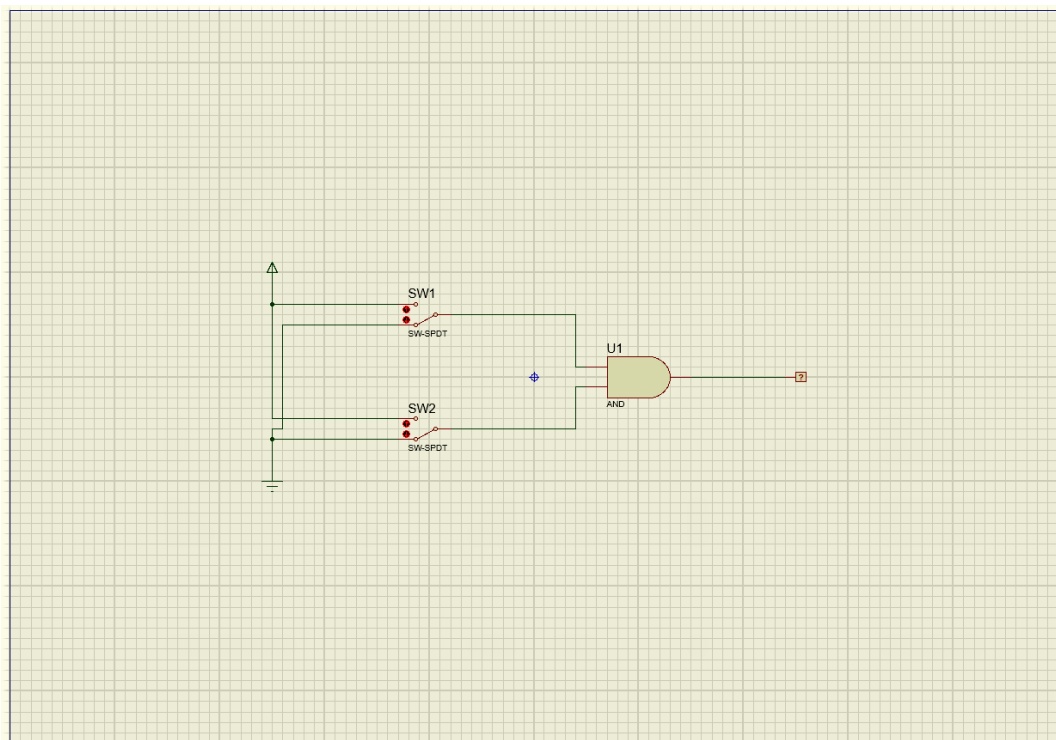

Picture 1.2. New logic gate combination

Experiment 2

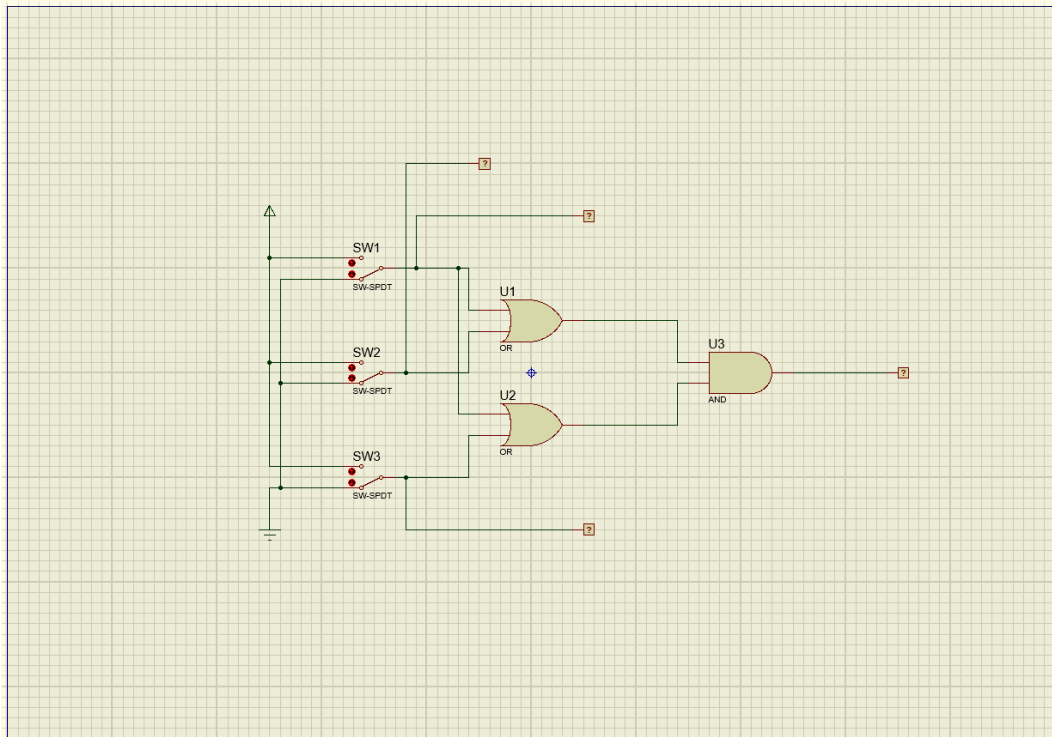

Picture 2.1. Logic gate combination

1. Boolean functions

$$F = ABC + AC$$

2. Truth table

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 |


3. Karnaugh map

| | | AB | | | |
|---|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| C | 0 | 0 | 0 | 1 | 1 |
| | 1 | 0 | 1 | 1 | 1 |

4. Boolean functions based on karnaugh map


$$A+BC$$

5. Logic gate combination based on new boolean functions

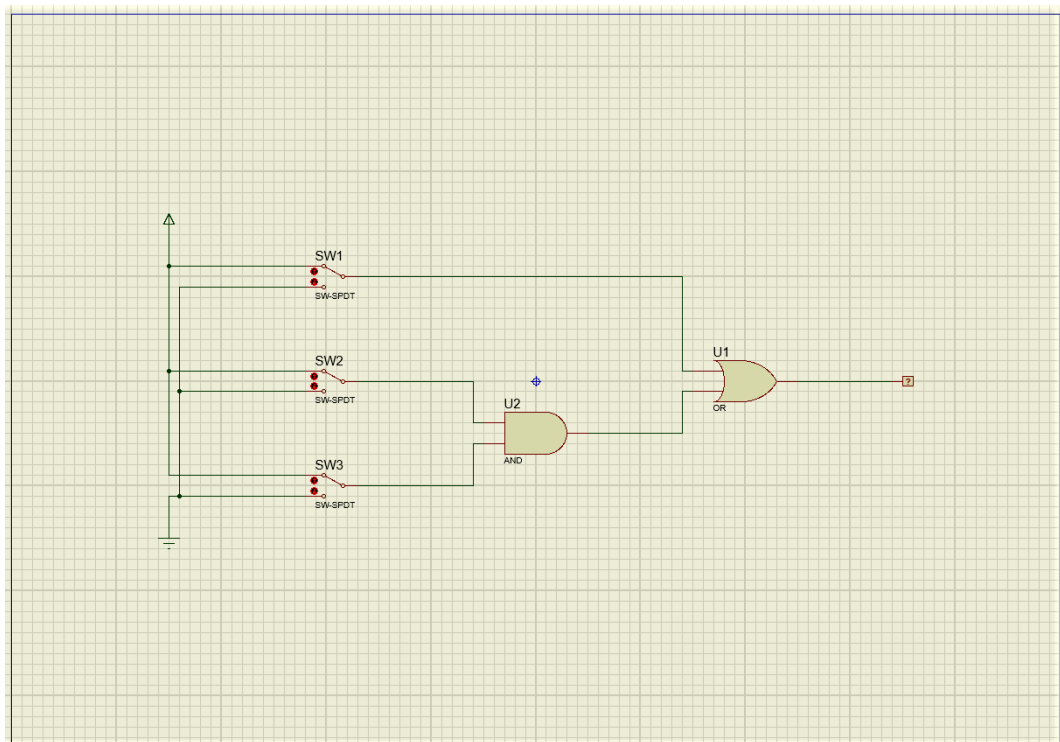

Picture 2.2. New logic gate combination

Experiment 3

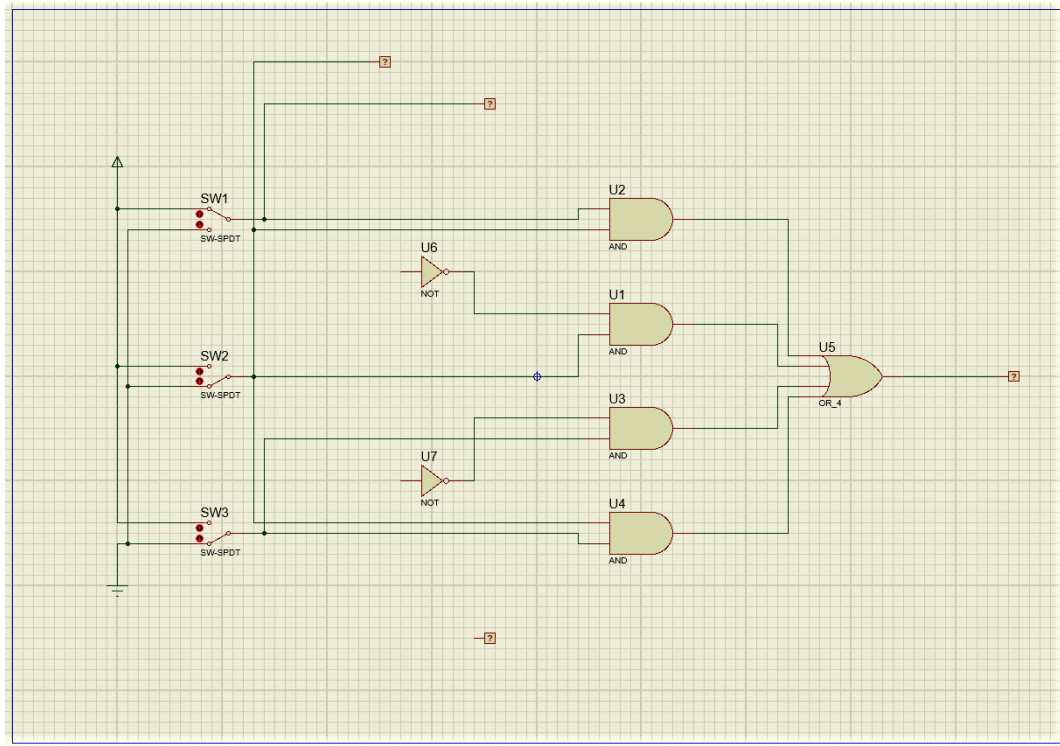

Picture 3.1. Logic gate combination

1. Boolean function

$$F = AB + A'B + B'C + BC$$

2. Truth table

| A | B | C | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 |


3. Karnaugh map

| | | AB | | | |
|---|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| C | 0 | 0 | 1 | 1 | 0 |
| | 1 | 1 | 1 | 1 | 1 |

4. Boolean functions based on karnaugh map

$$B+C$$

5. Logic gate combination based on new boolean functions

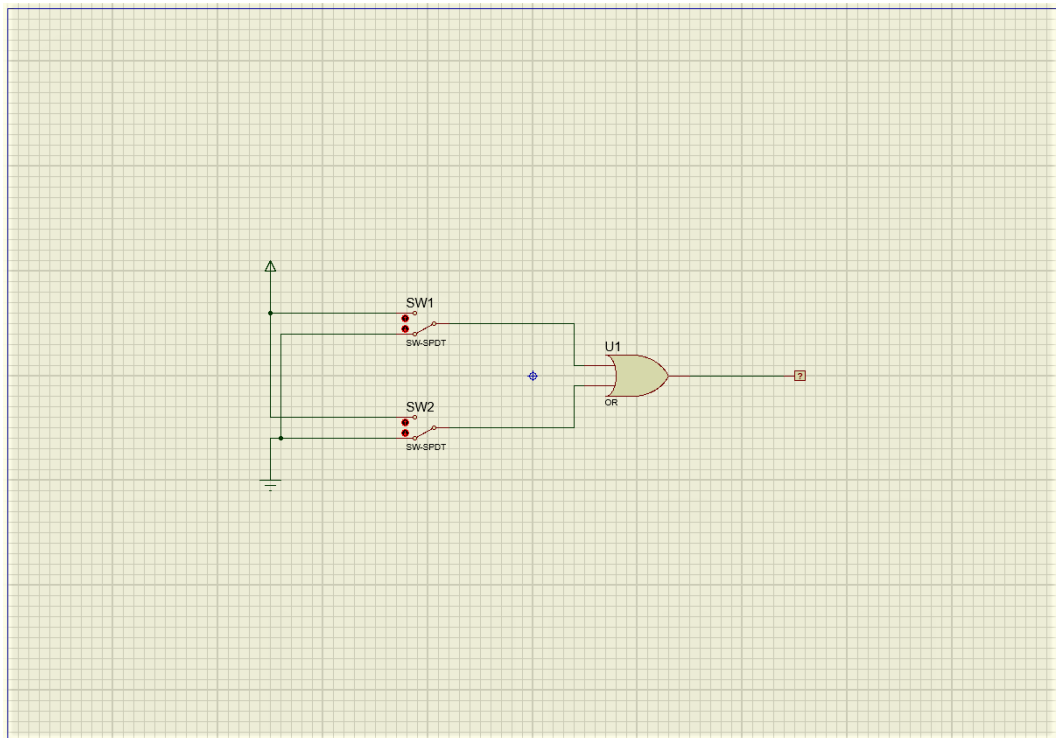

Picture 3.2. New logic gate combination