

DIGITAL SYSTEMS

PRACTICUM 12



By:

MUHAMMAD ROSYAD ADI PRATAMA


NIM: L200184044

INFORMATION TECHNOLOGY

FACULTY OF COMMUNICATION AND INFORMATICS

UNIVERSITY OF MUHAMMADIYAH SURAKARTA

Experiment 1

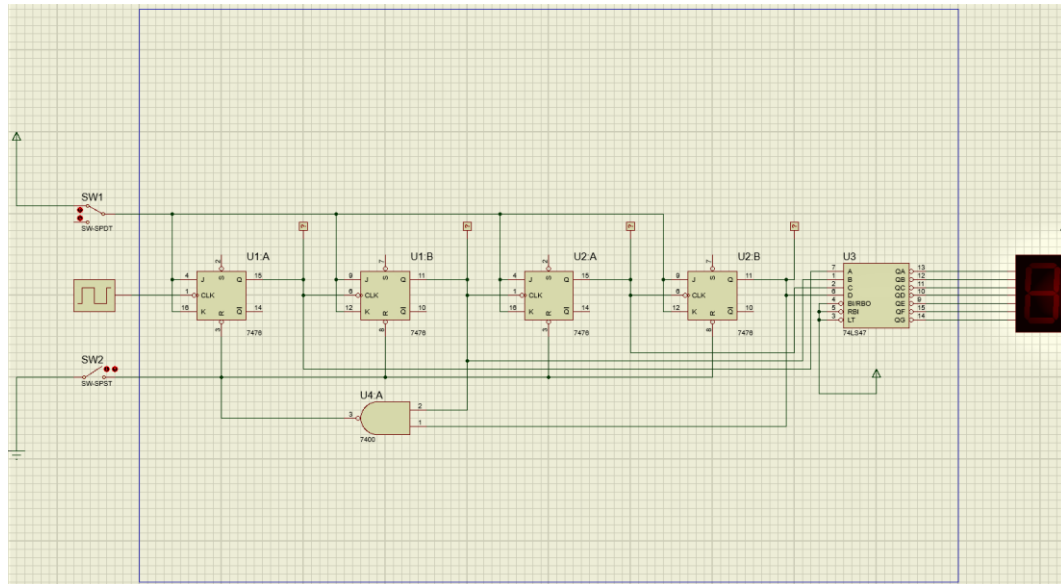


Picture 1.1. Modulus 10 and Decoder circuit

1. What is the output seen in the seven segment?

Answer: The seven segment output is in the form of calculations from 1 to 9.

Experiment 2

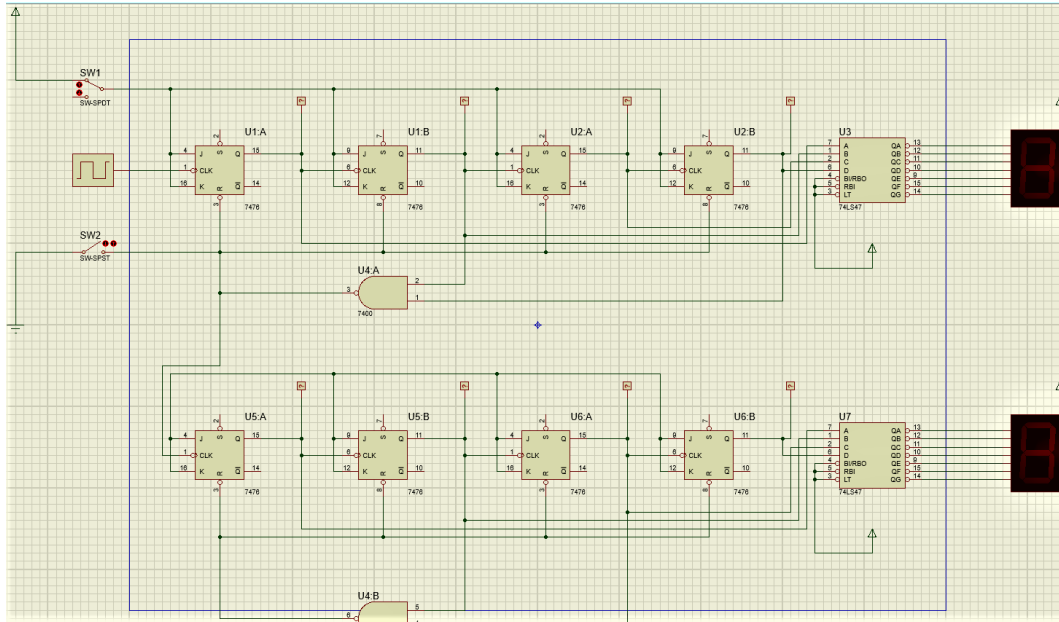

Picture 2.1. Modulus 6 and Decoder circuit

1. What is the clock function in the series above?
Answer: To determine the speed of calculation.
2. Explain the usefulness of the SPDT Switch in the series above!
Answer: To check the value of the decoder.
3. Explain the usefulness of the SPST Switch in the series above!
Answer: To stop counting.