

INFORMATION TECHNOLOGY
UNIVERSITY OF MUHAMMADIYAH SURAKARTA
DIGITAL SYSTEMS
4th PRACTICE



By:
MUHAMMAD ROSYAD ADI PRATAMA
NIM: L200184044

Experiment 1

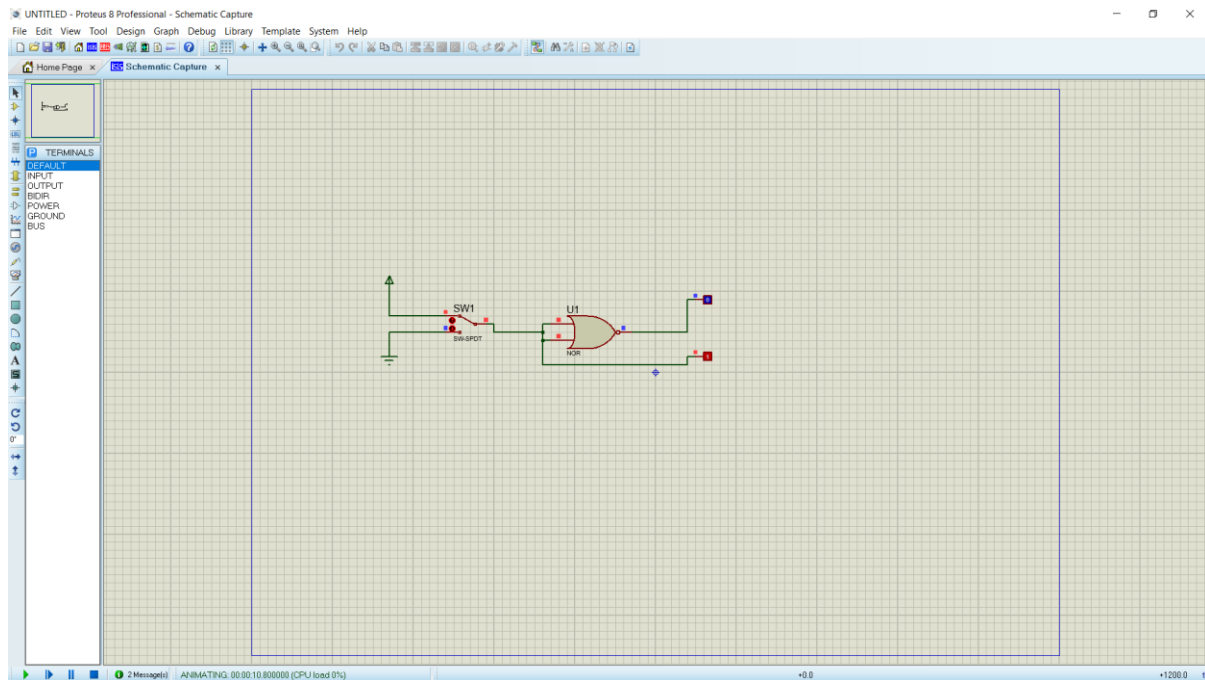


Image 1.1. Gate 1 variation

1. Truth table

SW1	L2	L1
0	0	1
1	1	0

2. Time diagram

L1



L2



3. Conclusion

The NOR gate in Image 1.1 forms the logic of the NOT gate

Experiment 2

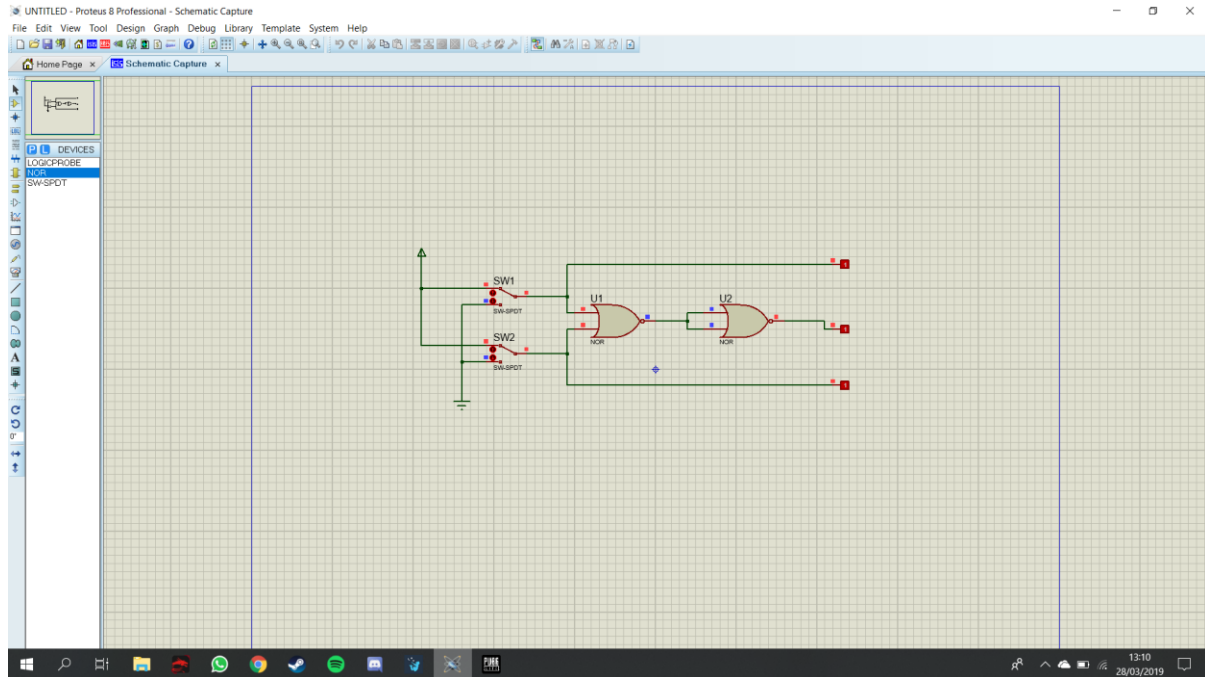


Image 2.1. Gate 2 variation

1. Truth table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	1

2. Time diagram


L1



L2



L3

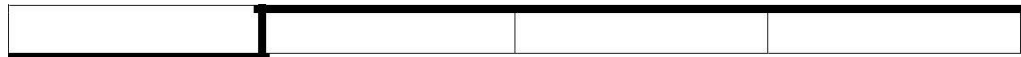

3. Conclusion

The NOR gate in Image 2.1 forms the logic of the OR gate

Experiment 3

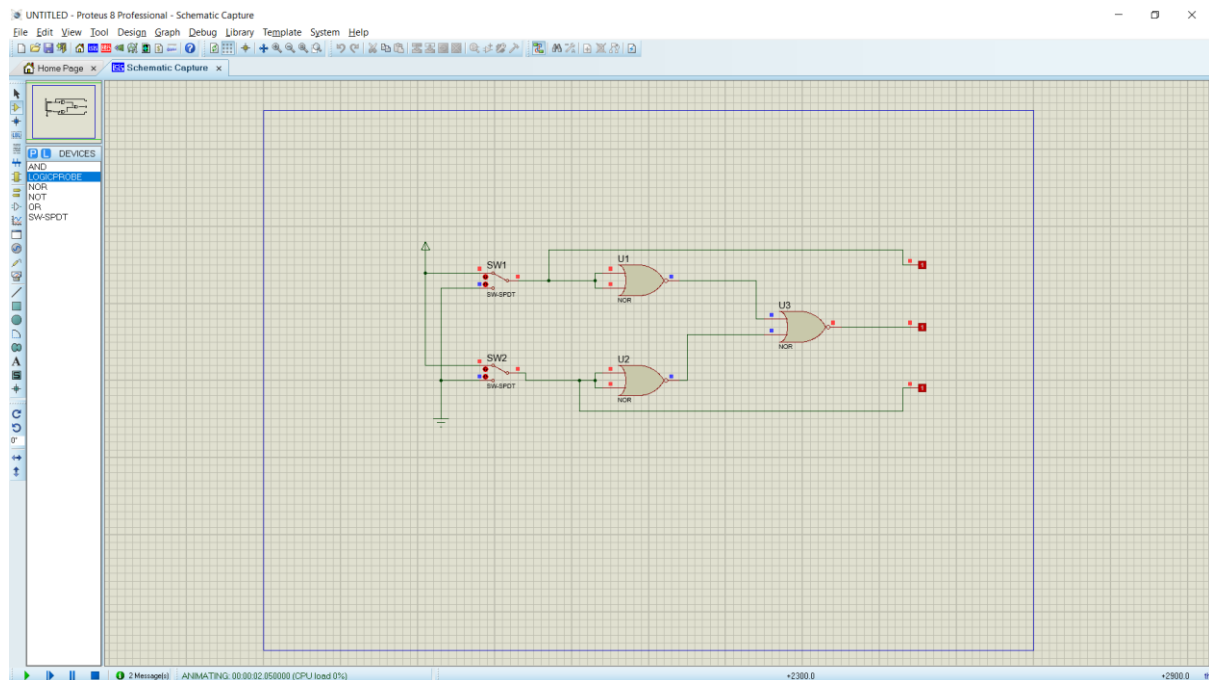


Image 3.1. Gate 3 variation

1. Truth table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	0
0	1	0	1	0
1	1	1	1	1

2. Time diagram

L1



L2



L3



3. Conclusion

The NOR gate in Image 3.1 forms the logic of the AND gate

Experiment 4

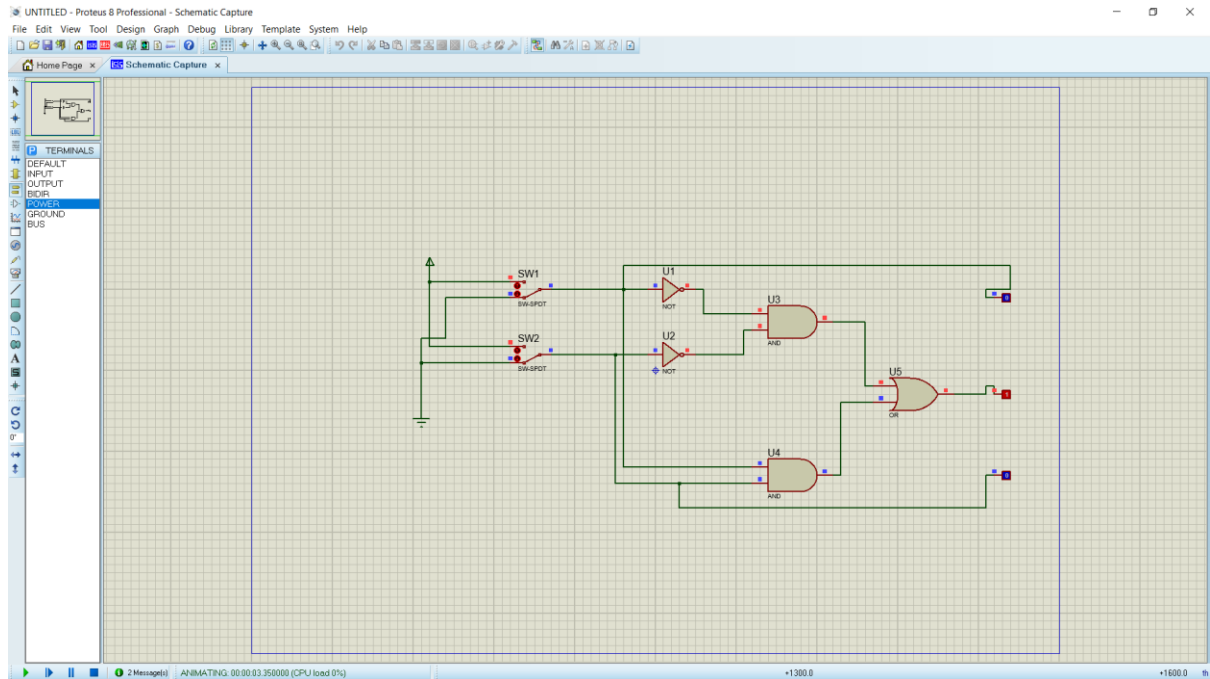


Image 4.1. Gate 4 variation

1. Truth table

SW1	SW2	L1	L2	L3
0	0	0	0	1
1	0	1	0	0
0	1	0	1	0
1	1	1	1	1

2. Time Diagram

L1



L2



3. Conclusion

- The NOR gate in Image 4.1 forms the logic of the XNOR gate

Experiment 5

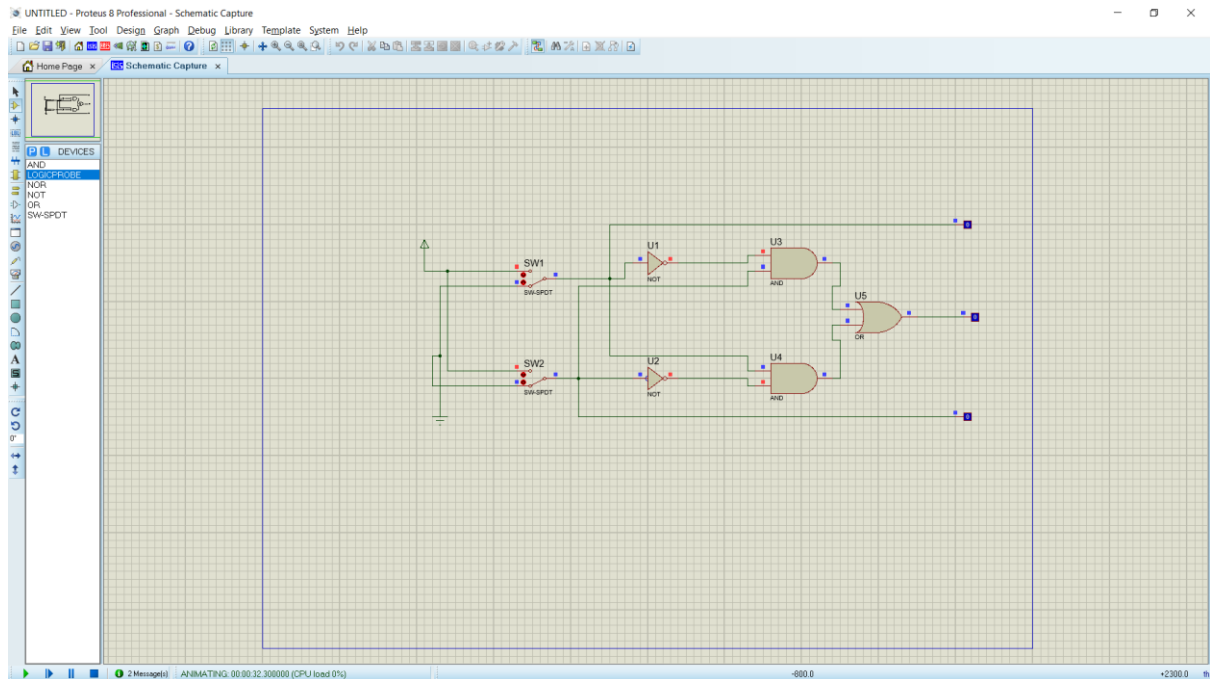


Image 5.1. Gate 5 variation

1. Truth Table

SW1	SW2	L1	L2	L3
0	0	0	0	0
1	0	1	0	1
0	1	0	1	1
1	1	1	1	0

2. Diagram Waktu


L1



L2



L3

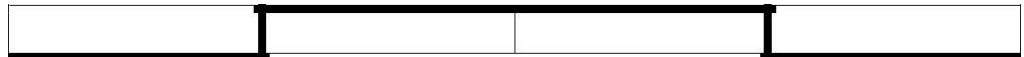

3. Conclusion

The NOR gate in Image 4.1 forms the logic of the XOR gate

Additional Experiment 1

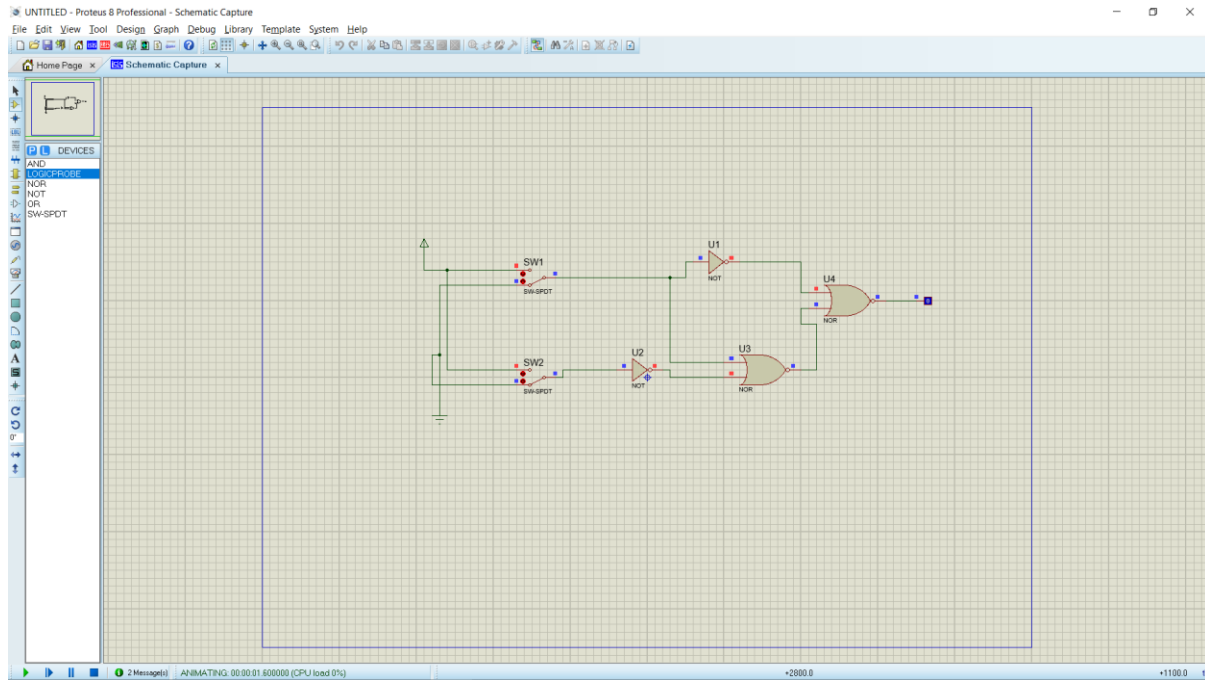


Image 6.1. Set of gate

1. Truth Table

X	Y	F
0	0	0
0	1	0
1	0	1
1	1	1

2. Time Diagram

L1



3. Boolean Function

$$F = \neg(\neg X + \neg(X + \neg Y)) = X(X + \neg Y)$$

Additional Experiment 2

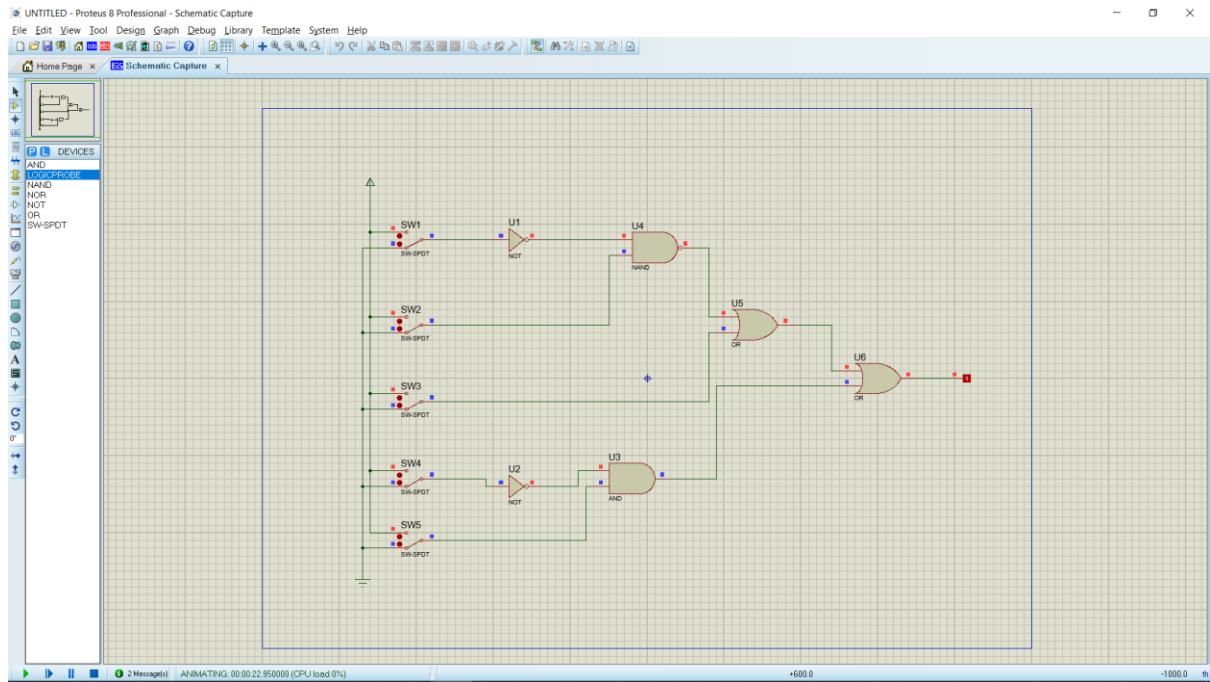


Image 7.1. Set of gate for boolean function $F = (\neg(\neg A.B) + C) + (\neg D.E)$