# DIGITAL SYSTEMS PRACTICUM 6



#### By:

#### MUHAMMAD ROSYAD ADI PRATAMA

NIM: L200184044


# INFORMATION TECHNOLOGY FACULTY OF COMMUNICATION AND INFORMATICS UNIVERSITY OF MUHAMMADIYAH SURAKARTA

#### 1. Karnaugh map

		AB				
		00 01 11 10				
CD	00	0	0	0	0	
	01	1	1	1	0	
	11	0	1	1	1	
	10	0	0	0	0	

# 2. Boolean function

$$F = A'C'D + BD + ACD$$

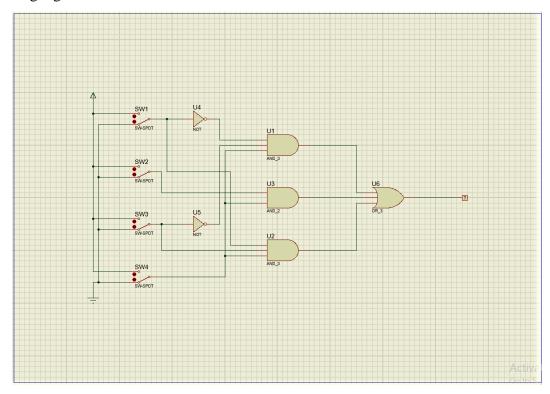

Picture 1.1. Logic gate combination based on boolean function


#### 1. Karnaugh map

		AB				
		00 01 11 10				
CD	00	1	0	0	1	
	01	0	1	1	0	
	11	0	1	1	0	
	10	1	0	0	1	


# 2. Boolean Function

a. 
$$F = BD + B'D' (AND-OR)$$

b. 
$$F = B'D + BD'$$
 (OR-AND)

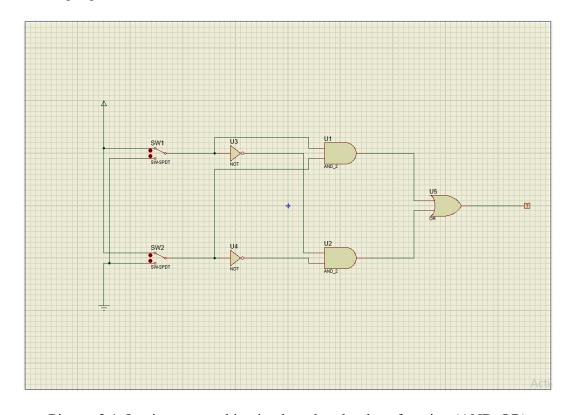

Picture 2.1. Logic gate combination based on boolean function (AND-OR)

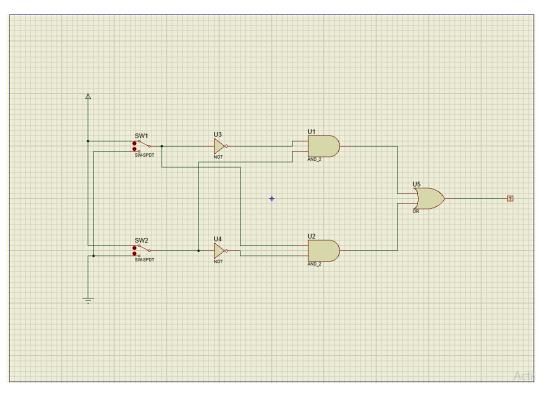

Picture 2.2. Logic gate combination based on boolean function (OR-AND)

1. Boolean Function


$$F = XYZ + XYZ' + XY'Z + X'YZ + X'YZ' + XY'Z' + X'Y'Z'$$

2. Karnaugh map

		XY			
		00	01	11	10
Z	0	1	1	1	1
	1	0	1	1	1

3. Simplification of boolean function

$$F = Z' + Y + X$$

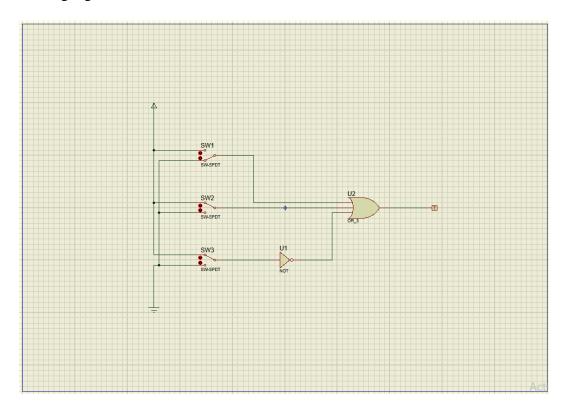

Picture 3.1. Logic gate combination based on simplification of boolean function

1. Boolean function


$$F = AD' + ABC + ABC' + BCD + BC'D' + AB'CD'$$

2. Karnaugh map

		AB			
		00 01 11 10			
CD	00	0	1	1	1
	01	0	0	1	0
	11	0	1	1	0
	10	0	0	1	1

3. Simplification of boolean function

$$F = AB + AD' + B$$

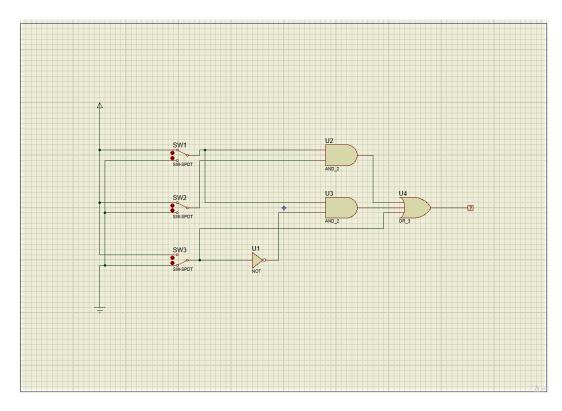

Picture 4.1. Logic gate combination based on simplification of bolean function

1. Table of boolean function


A	В	C	D	F
0	0	0	0	1
1	0	0	0	0
0	1	0	0	0
1	1	0	0	1
0	0	1	0	1
1	0	1	0	1
0	1	1	0	0
1	1	1	0	0
0	0	0	1	1
1	0	0	1	1
0	1	0	1	0
1	1	0	1	1
0	0	1	1	1
1	0	1	1	0
0	1	1	1	1
1	1	1	1	0

2. Karnaugh Map

		AB				
		00 01 11 10				
CD	00	1	0	1	0	
	01	1	0	1	1	
	11	1	1	0	0	
	10	1	0	0	1	

3. Simplification of boolean function

$$F = A'B' + B' + A'CD + C'$$

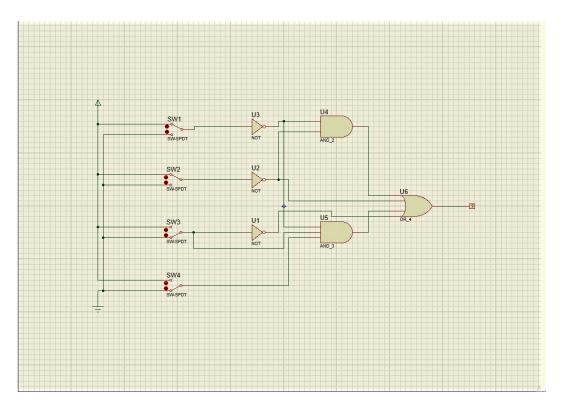

Picture 5.1. Logic gate combination based on simplification of boolean function